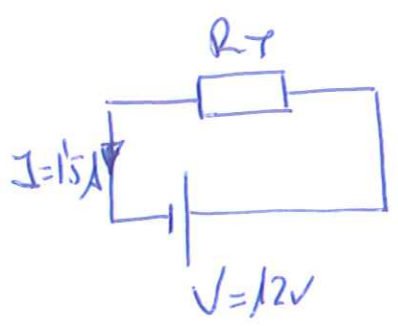


6) a) $R_T = \frac{U}{I}$

$\begin{cases} I = 1.5A \\ U = 12V \end{cases}$


1



$R_T = \frac{12V}{1.5A} = 8\Omega$

$R_T = 8\Omega$

Circuitos Serie

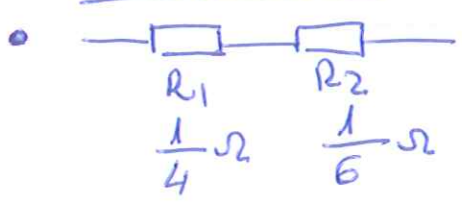

$R_S = R_1 + R_2 = \frac{1}{4}\Omega + \frac{1}{6}\Omega = \frac{3\Omega}{12} + \frac{2\Omega}{12} = \frac{5}{12}\Omega$

$R_S = \frac{5}{12}\Omega = 0.41\Omega$

$R_S = 0.41\Omega = \frac{5}{12}\Omega$

R paralelos

$\frac{1}{R_P} = \frac{1}{R_5} + \frac{1}{R_3} = \frac{1}{\frac{5}{12}} + \frac{1}{\frac{8}{5}} = \frac{12}{5} + \frac{8}{5} = \frac{20}{5} = 4\Omega$

$\frac{1}{R_P} = 4\Omega \Rightarrow R_P = \frac{1}{4}\Omega = 0.25\Omega$

$R_P = 0.25\Omega = \frac{1}{4}\Omega$

$R_4 = 8\Omega - 0.25 = 7.75\Omega$

$R_4 = 7.75\Omega$

b)

$R_4 \Rightarrow I_{R_4} = \frac{U_{R_4}}{R_4} \Rightarrow I_{\text{del circuito}} = I_{R_4} = 1.5A$

$R_3 \Rightarrow I_{R_3} = \frac{U_{R_3}}{R_3} =$

$R_2 \Rightarrow I_{R_2} = \frac{U_{R_2}}{R_2}$

$R_1 \Rightarrow I_{R_1} = \frac{U_{R_1}}{R_1}$

© Tensiones

2

$$V_{R4} = R_4 \cdot I = 7'75 \Omega \cdot 1'5 A = 11'625 V.$$

$$V_{R4} = 11'625 V$$

$$V_{R \text{ paralelo}} \Rightarrow ??$$


$$V_T = V_{R \text{ paralelo}} + V_{R4}$$

$$12 V = V_{R \text{ paralelo}} + 11'625 V$$

$$12 V - 11'625 V = V_{R \text{ paralelo}} \Rightarrow V_{R \text{ paralelo}} = 0'375 V$$

$$V_{R \text{ paralelo}} = V_{R3} = 0'375 V \quad \text{Al ser un circuito paralelo}$$

ejemplo:

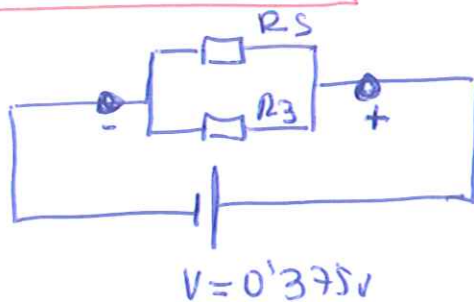

$$V_{R5} = V_{R3} = V = 0'375 V$$

$$V_{R5} = V_{R3} = 0'375 V.$$

$$V_{R5} = I_{\text{serie}} \cdot R_{\text{serie}}. \quad (\text{despejamos } I_{\text{serie}})$$

$$I_{\text{serie}} = \frac{V_{R5}}{R_5} = \frac{0'375 V}{0'4 \Omega} = 0'9 A.$$


(inicio problema)

En un circuito serie:

$$I_{\text{serie}} = I_{R1} = I_{R2} = 0'9 A.$$

En un circuito paralelo se reparten las corrientes

3

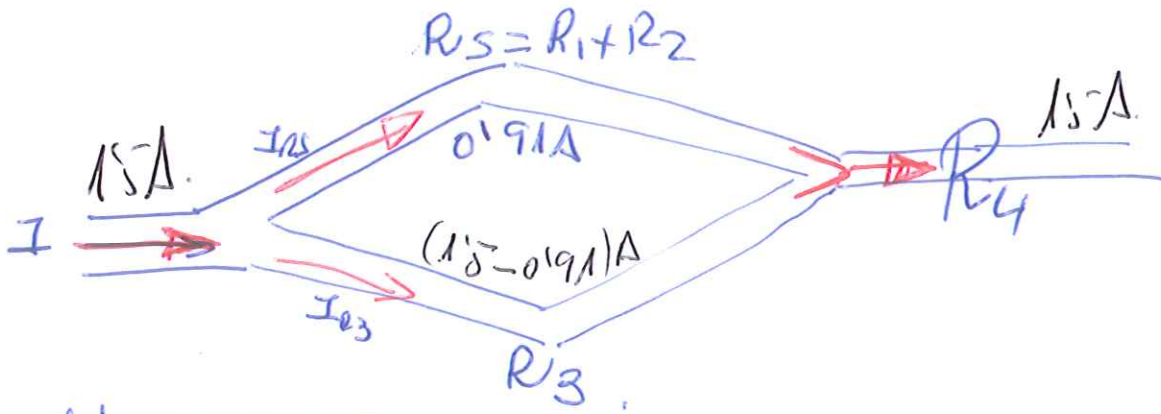

Paralelo	<u>Teoría</u>
$I = I_{R1} + I_{R3}$	
Serie	
$I = I_{R4}$	

$$I = I_{R1} + I_{R3}$$

$$1.5A = 0.91A + I_{R3}$$

$$I_{R3} = 1.5A - 0.91A = 0.59A$$

$$I_{R3} = 0.59A$$

Resumen

$$I = 1.5A$$

$$I_{R1} = 0.91A$$

$$\begin{cases} I_{R1} = V_{R1} / R1 \\ I_{R2} = V_{R2} / R2 \end{cases} \Rightarrow \text{despejando } V_{R1} \text{ y } V_{R2}$$

$$I_{R3} = 0.59A$$

$$I_{R4} = I = 1.5A$$

Tensiones - V_{R1} y V_{R2}

$$V_{R1} = R1 \cdot I_{R1} = \frac{1}{4} \Omega \cdot 0.91A = 0.2275V \quad (V_{R1} = 0.2275V)$$

$$V_{R2} = R2 \cdot I_{R2} = \frac{1}{6} \Omega \cdot 0.91A = 0.1516V \quad V_{R2} = 0.15V$$

$V_{\text{paralelo}} = \frac{V_{R1}}{2} \rightarrow 0.3775V$
correcto.